

# Contents

|          |                                                       |           |
|----------|-------------------------------------------------------|-----------|
| <b>1</b> | <b>Introduction</b>                                   | <b>1</b>  |
| 1.1      | Motivation . . . . .                                  | 1         |
| 1.2      | Basic definition . . . . .                            | 2         |
| <b>2</b> | <b>Components</b>                                     | <b>5</b>  |
| 2.1      | Semiconductor devices . . . . .                       | 5         |
| 2.1.1    | Diode . . . . .                                       | 6         |
| 2.1.2    | MOSFET transistor . . . . .                           | 7         |
| 2.2      | Passive component . . . . .                           | 10        |
| 2.2.1    | Inductor . . . . .                                    | 10        |
| 2.2.2    | Capacitor . . . . .                                   | 10        |
| 2.2.3    | Transformer . . . . .                                 | 13        |
| 2.3      | Connections . . . . .                                 | 18        |
| 2.4      | Line Impedance Stabilization Network . . . . .        | 22        |
| <b>3</b> | <b>Non isolated converters</b>                        | <b>25</b> |
| 3.1      | Introduction . . . . .                                | 25        |
| 3.2      | Boost converter - basic operation . . . . .           | 25        |
| 3.2.1    | Continuous mode . . . . .                             | 27        |
| 3.2.2    | Boundary conduction mode . . . . .                    | 31        |
| 3.2.3    | Discontinuous mode . . . . .                          | 35        |
| 3.2.4    | Output voltage ripple . . . . .                       | 37        |
| 3.3      | EMI propagation paths . . . . .                       | 38        |
| 3.3.1    | Transistor capacitance . . . . .                      | 41        |
| 3.3.2    | Diode capacitance . . . . .                           | 42        |
| 3.3.3    | Parasitic capacitance connected to MOSFET terminals . | 44        |

---

|          |                                                           |            |
|----------|-----------------------------------------------------------|------------|
| 3.3.4    | Parasitic inductance in transistor branch . . . . .       | 44         |
| 3.3.5    | Driver . . . . .                                          | 46         |
| 3.3.6    | Parasitic inductance in diode branch . . . . .            | 47         |
| 3.3.7    | Inductor . . . . .                                        | 47         |
| 3.4      | Conclusion . . . . .                                      | 49         |
| <b>4</b> | <b>Flyback converter</b>                                  | <b>53</b>  |
| 4.1      | Introduction - basic operation . . . . .                  | 53         |
| 4.1.1    | Continuous current mode . . . . .                         | 55         |
| 4.1.2    | Boundary current conduction mode . . . . .                | 61         |
| 4.1.3    | Discontinuous current mode . . . . .                      | 64         |
| 4.2      | EMI propagation paths . . . . .                           | 68         |
| 4.2.1    | Transistor . . . . .                                      | 71         |
| 4.2.2    | Diode . . . . .                                           | 74         |
| 4.2.3    | Transformer . . . . .                                     | 76         |
| 4.2.4    | Simplified model for ringing frequency identification . . | 81         |
| <b>5</b> | <b>Isolated converters</b>                                | <b>83</b>  |
| 5.1      | Introduction . . . . .                                    | 83         |
| 5.2      | Full bride converter – basic operation . . . . .          | 83         |
| 5.2.1    | Continuous mode . . . . .                                 | 84         |
| 5.2.2    | Boundary conduction mode . . . . .                        | 87         |
| 5.3      | EMI propagation paths . . . . .                           | 90         |
| 5.3.1    | Transformer . . . . .                                     | 93         |
| 5.3.2    | Semiconductors . . . . .                                  | 97         |
| <b>6</b> | <b>Summary</b>                                            | <b>103</b> |
|          | List of Symbols . . . . .                                 | 104        |
| <b>7</b> | <b>Appendix</b>                                           | <b>113</b> |
|          | List of Figures                                           | 115        |