

Contents

Preface8

Chapter 1 • Introduction10

1.1 Overview10

1.2 Types of 555 timer chips10

1.3 555 timer chip specifications.10

1.3.1 The NE555P chip10

Chapter 2 • Operation of the 555 Timer Chip.13

2.1 Block Diagram.13

2.2 Astable Circuit Operation13

2.2.1 Using a nomogram16

2.2.2 555 astable online calculator17

2.2.3 Astable circuit with duty cycle less than or equal to 50%19

2.2.4 Astable circuit with duty cycle adjustable from 0% to 100%.21

2.2.5 Component values for required frequency and duty cycle range22

2.2.6 A simpler circuit for 50% duty cycle24

2.3 Monostable Circuit Operation26

2.3.1 Using a nomogram28

2.3.2 555 monostable online calculator28

2.4 Bistable Circuit Operation29

2.4.1 Using the Reset input.29

2.4.2 Using pins 2 and 6.30

2.5 Online Calculator Program for Designing 555 Astable and Monostable Circuits31

2.6 555 Timer Output Current31

2.7 Driving Heavy Loads32

2.7.1 Using bipolar transistors.32

2.7.2 Using a MOSFET transistor32

2.7.3 Using a relay33

Chapter 3 • 555 Timer Projects34

3.1 Overview34

3.2 Project 1: Flashing LED34

3.3 Project 2: Police Car Emergency Lights — Alternately Flashing Two LEDs 36

3.4 Project 3: Changing the LED Flash Rate 38

3.5 Project 4: Changing the LED Brightness 40

3.6 Project 5: Touch Sensor On/Off Switch. 43

3.7 Project 6: Pushbutton On/Off switch 45

3.8 Project 7: Switch-Off Delay. 46

3.9 Project 8: Switch-On Delay. 48

3.10 Project 9: Light-dependent Sound 49

3.11 Project 10: Darkness Sensor. 52

3.12 Project 11: Light Sensor 54

3.13 Project 12: Astable Frequency Generator 55

3.14 Project 13: Tone Burst Generator. 57

3.15 Project 14: Drawer/Cupboard Light Switch 59

3.16 Project 15: Long Duration Timer with Decade Counter 60

3.17 Project 16: Long Duration Timer with Binary Counter. 63

3.18 Project 17: Chasing LEDs 64

3.19 Project 18: LED Roulette Game 67

3.20 Project 19: Simple Traffic Lights Controller 69

3.21 Project 20: Professional Traffic Lights Controller 71

3.22 Project 21: Sine Wave Output 73

3.23 Project 22: Continuity Tester. 76

3.24 Project 23: Simple Logic Probe 77

3.25 Project 24: Electronic Lock — Bistable Mode 79

3.26 Project 25: Electronic Lock — Monostable Mode. 81

3.27 Project 26: Extending the Monostable Duration — Retriggering 82

3.28 Project 27: Switch Contact Debouncing 84

3.29 Project 28: Schmitt Trigger Circuit 85

3.30 Project 29: Monophonic Toy Electronic Organ 87

3.31 Project 30: 8-Tone Electronic Organ 90

3.32 Project 31: Multiple Sensor Alarm Circuit 92

3.33 Project 32: Monostable with Selectable Durations 93

3.34 Project 33: Electronic Metronome95

3.35 DC Voltage Multipliers97

 3.35.1 Project 34: DC Voltage Doubler.97

 3.35.2 Project 35: DC Voltage Tripler.99

 3.35.3 Project 36: DC Voltage Quadrupler100

3.36 Project 37: 7-segment LED Counter.100

3.37 Project 38: 2-digit, 7-segment LED Counter105

3.38 Project 39: LED Dice106

3.39 Project 40: 7-segment LED Dice108

3.40 Project 41: DC Motor Control111

3.41 Project 42: Servo Motor Control114

3.42 Project 43: Temperature Alarm Circuit116

3.43 Project 44: Temperature Controller118

3.44 Project 45: DC Motor H-bridge Control119

3.45 Project 46: Fastest Finger First Quiz Circuit — Two Participants.122

3.46 Project 47: Fastest Finger First Quiz Circuit — Six Participants in Three Groups. .124

3.47 Using The 555 Timer Control Pin126

 3.47.1 Project 48: Voltage Controlled Oscillator126

 3.47.2 Project 49: Simple British Police Siren128

3.48 Project 50: More Elaborate British Police Siren130

Chapter 4 • The 556 and 558 Timer ICs.132

 4.1 Overview132

 4.2 The 556 Timer IC132

 4.3 The 558 Timer IC132

Chapter 5 • The CMOS Version of the 555 Timer136

 5.1 Overview136

 5.2 The LMC555 CMOS Timer136

Chapter 6 • List of Components Used in the Projects138

Appendix • Bibliography.139

Index140