

Contents

1	Continuous-Time Systems	1
1.1	Relations in the Time Domain	1
1.2	Relations in the Frequency Domain	2
1.2.1	The Laplace Transform	3
1.2.2	The Fourier Transform	5
1.3	Transfer Functions	7
1.4	Allpass Transfer Function	13
1.5	The Squared Magnitude of Transfer Functions	15
2	Analog Filters	19
2.1	Filter Approximation	19
2.2	Butterworth Filters	23
2.3	Chebyshev Filters	27
2.4	Inverse Chebyshev Filters	33
2.5	Elliptic Filters	35
2.5.1	Properties of the Jacobian Elliptic Function	36
2.5.2	Elliptic Filter Design	40
2.5.3	Calculation of the Poles and Zeros	44
2.6	Bessel Filters	50
2.7	Filter Transformations	57
2.7.1	Low-Pass High-Pass Transformation	59
2.7.2	Low-Pass Bandpass Transformation	60
2.7.3	Low-Pass Bandstop Transformation	61
2.8	Passive Filter Networks	64
2.8.1	The Lossless Two-port	64
2.8.2	Two-port Equations	69
2.8.3	Network Configurations	72
2.8.4	Ladder Filters	74
2.8.5	Lattice Filter	77

3	Discrete-Time Systems	85
3.1	Discrete-Time Convolution	86
3.2	Relations in the Frequency Domain	88
3.3	The z -Transform	94
3.3.1	Definition of the z -Transform	94
3.3.2	Properties of the z -Transform	95
3.4	Stability Criterion in the Time Domain	101
3.5	Further Relations of Interest	102
3.5.1	Magnitude at $\omega = 0$ and $\omega = \pi/T$	102
3.5.2	Parseval's Theorem	103
3.5.3	Group Delay Calculation in the z -Domain	104
4	Sampling Theorem	107
4.1	Introduction	107
4.2	Sampling	107
4.3	Band-Limited Signals	109
4.4	Signal Conversion	110
4.4.1	Analog-to-Digital Conversion	110
4.4.2	Digital-to-Analog Conversion	112
4.4.2.1	Implementational Aspects	112
4.4.2.2	Mathematical Analysis of the D/A Conversion Process	113
4.4.2.3	Storage and Payout of Analog Signals	115
4.4.2.4	Ideal Signal Reconstruction	118
5	Filter Structures	123
5.1	Graphical Representation of Discrete-Time Networks	123
5.1.1	Block diagram and flowgraph	123
5.1.2	Realisability	126
5.2	FIR Filters	127
5.2.1	The Basic Structure of FIR Filters	127
5.2.2	Magnitude Response	132
5.2.3	Reciprocal Conjugate Zeros	133
5.2.4	Phase Response	135
5.2.5	Group Delay	137
5.2.6	Linear-Phase Filters	140
5.3	IIR Filters	146
5.3.1	An Introductory Example	146
5.3.2	Direct Form Filters	147
5.3.3	Poles and Zeros	150
5.3.4	Stability Considerations in the Frequency Domain	154
5.4	State-Space Structures	156
5.5	The Normal Form	161

5.6	Digital Ladder Filters	163
5.6.1	Kirchhoff Ladder Filters	163
5.6.2	Wave Digital Filters	169
5.6.2.1	Wave Parameters.	169
5.6.2.2	Decomposition of the Analog Reference Network into One-Ports and Multi-Ports	175
5.6.2.3	The Reflectance of the Capacitor and the Inductor	179
5.6.2.4	The Role of the Bilinear Transform.	182
5.6.2.5	Observance of the Realisability Condition . . .	184
5.6.2.6	Second-Order Wave Digital Filter Block	187
5.7	Allpass Filters	189
5.7.1	Allpass Transfer Function	191
5.7.2	Allpass Filter Structures	196
5.7.2.1	Direct form.	196
5.7.2.2	Multiplier Extraction	198
5.7.2.3	Wave Digital Filter	202
5.7.3	Applications	210
5.7.3.1	The Gray And Markel Filter Structure.	211
5.7.3.2	The Digital Lattice Filter	215
5.7.3.3	Notch Filter	220
5.7.3.4	Equalisers.	225
5.7.3.5	Approximately Linear-Phase Filters.	228
5.7.3.6	Filter Bank Structure	232
5.7.3.7	90-Degree Phase Shift	234
5.7.3.8	Fractional Delay	237
5.8	Software Implementation of Digital Filter Algorithms.	240
5.8.1	State-Space Structures.	241
5.8.2	Program Flow	244
5.8.3	Second-Order Filter Blocks	246
5.8.4	FIR Filters.	254
5.8.5	Fixed-Point Implementation.	257
6	Design of IIR Filters.	259
6.1	Introduction	259
6.2	Preservation Theorem of the Convolution	260
6.3	Approximation in the Time Domain	263
6.3.1	Continuous-Time Filter Responses	263
6.3.2	Sampling the Analog Filter Responses	266
6.3.3	Impulse-Invariant Design	270
6.3.4	Step-Invariant Design	276
6.3.5	Ramp-Invariant Design	279
6.3.6	Summary.	283

6.4	Approximation in the Frequency Domain	284
6.4.1	Difference Method	285
6.4.2	Bilinear Transform	289
6.4.3	Practical Filter Design Using the Bilinear Transform . . .	294
6.4.4	IIR Filters with Bessel Characteristics	298
6.5	Allpass Filter Design	301
6.5.1	Interpolation	305
6.5.2	Least Mean Square Design	313
6.5.3	Quasi-Equiripple Design	318
6.5.4	True Equiripple Design	320
6.5.5	MAXFLAT Design	324
7	Design of FIR Filters	329
7.1	Introduction	329
7.2	Linear-Phase Filters	330
7.3	Frequency Sampling	333
7.4	Minimisation of the Mean-Square Error	340
7.4.1	Direct Solution	343
7.4.2	The Window Method	350
7.4.3	Arbitrary Magnitude Responses	355
7.5	Chebyshev Approximation	359
7.5.1	The Remez Exchange Algorithm	359
7.5.2	Polynomial Interpolation	362
7.5.3	Introduction of a Weighting Function	366
7.5.4	Case 2, 3 and 4 Filters	369
7.5.5	Minimum-Phase FIR Filters	371
7.6	Maximally Flat (MAXFLAT) Design	375
8	Effects of Finite Register Length	383
8.1	Classification of the Effects	383
8.2	Number Representation	383
8.2.1	Fixed-Point Numbers	384
8.2.2	Floating-Point Numbers	387
8.3	Quantisation	389
8.3.1	Fixed-Point Numbers	389
8.3.2	Floating-Point Numbers	394
8.4	System Noise Behaviour	397
8.4.1	Signal-to-Noise Ratio	397
8.4.2	Noise Filtering by LSI Systems	399
8.4.3	Optimum Use of the Dynamic Range	401
8.5	Noise Optimisation with Fixed-Point Arithmetic	403
8.5.1	Noise Behaviour of First- and Second-Order Filter Blocks	403
8.5.2	Shaping of the Noise Spectrum	411
8.5.3	Noise in a Cascade of Second-Order Filter Blocks	416

8.6	Finite Coefficient Wordlength	420
8.6.1	Coefficient Sensitivity	421
8.6.2	Graphical Representation of the Pole Density	423
8.6.3	Increased Pole Density at Low and High Frequencies	428
8.6.4	Further Remarks Concerning Coefficient Sensitivity. . .	433
8.6.5	A Concluding Example.	434
8.7	Limit Cycles	437
8.7.1	Nonlinearities in Actual Implementations	438
8.7.2	Stability of the Linear Filter	440
8.7.3	Stability with Quantisation and Overflow Correction	445
8.7.4	A Constructive Approach for the Determination of Stability	446
8.7.4.1	The Linear System	446
8.7.4.2	Stability of the Nonlinear System	448
8.7.5	A Search Algorithm in the State Plane	460
8.7.6	Summary.	467
9	Oversampling and Noise Shaping	469
9.1	D/A Conversion	469
9.1.1	Upsampling and Interpolation	470
9.1.2	The CIC Interpolator Filter	474
9.1.3	Noise Filtering	479
9.1.4	Noise Shaping	481
9.2	A/D Conversion	483
9.2.1	Oversampling	483
9.2.2	Downsampling and Decimation	484
9.2.3	CIC Decimation Filter	486
9.2.4	Noise Filtering	487
9.2.5	Oversampling $\Delta\Sigma$ Conversion	488
10	Appendix	493
10.1	Symbols and Abbreviations	493
10.2	References.	495
10.3	Filter Design Tables	498
10.4	Filter Design Routines.	513
	Index	523