

Contents

Preface — VII

Chapter 1

An overview of PSIM® — 1

- 1.1 Introduction — 1
- 1.2 PSIM software — 1
- 1.3 Licensing — 3
- 1.4 PSIM environment — 3
- 1.5 Version of PSIM and installed modules — 10
- 1.6 PSIM's help menu — 11

Chapter 2

Basics of PSIM — 16

- 2.1 Introduction — 16
- 2.2 Analysis of a simple resistive circuit — 16
- 2.3 Simulating the circuit — 35
- 2.4 Measurement of circuit current — 39
- 2.5 Calculation of power — 43
- 2.6 Voltage and current sensors — 46
- 2.7 Measurement with current flag and voltage flag — 51
- 2.8 Calculation of power using voltage/current flag — 54
- 2.9 Color of connections — 57
- 2.10 Exporting the drawn schematic — 62
- 2.11 Addition of text to the schematic — 63
- 2.12 Addition of project information to the schematic — 65
- 2.13 Saving the schematic — 67
- 2.14 Protection of schematic files with password — 70
- 2.15 Compatible files for older versions of PSIM — 73
- 2.16 Enabling and disabling a component — 74
- 2.17 Shortcut keys — 78
- 2.18 List of used elements — 80
- 2.19 Removing the grids — 81
- 2.20 Backup files — 84
- 2.21 Automatic code generation blocks — 85
- 2.22 Utilities menu — 88
- 2.23 Simulation control block — 100
- 2.24 Free-run mode — 109
- 2.25 Change of elements' values during the simulation — 116
- 2.26 AC and DC voltmeters and ammeters — 119

Chapter 3

Simview™ — 128

- 3.1 Introduction — **128**
- 3.2 A sample simulation — **128**
- 3.3 Addition of label to the waveforms — **134**
- 3.4 Changing the color of waveforms and addition of new axis to the graph — **136**
- 3.5 Splitting the window — **140**
- 3.6 Zoom in, zoom out, and move — **143**
- 3.7 Customizing the X- and Y-axes — **144**
- 3.8 Cursors — **146**
- 3.9 Calculation of average and root mean square — **151**
- 3.10 Calculation of power factor, active power, and apparent power — **153**
- 3.11 Calculation of total harmonic distortion — **155**
- 3.12 Fast Fourier transform analysis — **159**
- 3.13 Exporting the waveforms to Excel® and MATLAB® — **162**
- 3.14 Reading the exported file in MATLAB environment — **164**
- 3.15 Exporting the graphic file of waveforms — **166**

Chapter 4

PSIM's elements — 167

- 4.1 Introduction — **167**
- 4.2 Resistor, inductor, and capacitor — **167**
- 4.3 Saturable inductor block — **178**
- 4.4 Coupled inductor block — **179**
- 4.5 DC Load block — **188**
- 4.6 Nonlinear elements — **196**
- 4.7 Filters — **202**
- 4.8 Computational blocks — **207**
- 4.9 Transfer function block — **220**
- 4.10 Logic elements — **224**
- 4.11 Math function — **226**
- 4.12 Switches — **234**
- 4.13 Transformers — **243**
- 4.14 Op amp — **247**
- 4.15 IC models — **252**

Chapter 5**Simulation of power electronic converters — 254**

- 5.1 Introduction — **254**
- 5.2 Example 1: simulation of a simple RC circuit — **254**
- 5.3 Example 2: effect of capacitor value on output waveform — **258**
- 5.4 Example 3: nonlinear elements — **262**
- 5.5 Example 4: switching the MOSFET — **266**
- 5.6 Example 5: R_switch_on and R_switch_off — **272**
- 5.7 Example 6: MOSFET conduction loss — **286**
- 5.8 Example 7: calculation of total harmonic distortion — **289**
- 5.9 Example 8: THD block — **293**
- 5.10 Example 9: Math Function voltage source block — **298**
- 5.11 Example 10: Wattmeter block — **300**
- 5.12 Example 11: average power measurement in presence of harmonics — **307**
- 5.13 Example 12: VAR meter block — **310**
- 5.14 Example 13: reactive power calculation in presence of harmonics — **318**
- 5.15 Example 14: VA/power factor meter block — **323**
- 5.16 Example 15: half-wave rectifier — **333**
- 5.17 Example 16: measurement of source power and diode losses for half-wave rectifier circuit — **338**
- 5.18 Example 17: single-phase full-wave uncontrolled rectifier — **342**
- 5.19 Example 18: diode bridge block — **348**
- 5.20 Example 19: three-phase uncontrolled rectifier — **351**
- 5.21 Example 20: single-phase half-wave controlled rectifier — **358**
- 5.22 Example 21: single-phase full-wave controlled rectifier — **363**
- 5.23 Example 22: measurement of power factor for different triggering angles — **374**
- 5.24 Example 23: three-phase controlled rectifier — **380**
- 5.25 Example 24: buck converter — **388**
- 5.26 Example 25: effect of time step on edges of signals — **396**
- 5.27 Example 26: making subcircuit — **398**
- 5.28 Example 27: PWM generation with carrier PWM controller block — **407**
- 5.29 Example 28: efficiency of SEPIC converter — **409**
- 5.30 Example 29: limiter blocks — **419**
- 5.31 Example 30: frequency response of control to output voltage for buck converter — **424**
- 5.32 Example 31: frequency response of control to inductor current for buck converter — **432**
- 5.33 Example 32: frequency response of electric circuit — **433**

- 5.34 Example 33: frequency response of filters — **438**
- 5.35 Example 34: input impedance of buck converter — **442**
- 5.36 Example 35: output impedance of buck converter — **450**
- 5.37 Example 36: closed-loop control of buck converter — **459**
- 5.38 Example 37: closed-loop control of buck converter with simplified C code block — **468**
- 5.39 Example 38: multiplexer block — **472**
- 5.40 Example 39: simulation of flyback and push-pull converter — **474**
- 5.41 Example 40: single-phase inverter — **476**
- 5.42 Example 41: three-phase inverter — **484**
- 5.43 Example 42: cascaded inverters — **488**
- 5.44 Example 43: multilevel inverters and SV PWM block — **496**
- 5.45 Example 44: magnetic components — **499**
- 5.46 Example 45: code generation and thermal modules — **511**

Chapter 6

Electrical machines — 514

- 6.1 Introduction — **514**
- 6.2 Simulation of a loaded DC motor — **514**
- 6.3 Reference direction of mechanical systems — **519**
- 6.4 Measurement of motor efficiency — **521**
- 6.5 Generator simulation — **522**
- 6.6 Efficiency of generator — **528**

Chapter 7

SimCoupler™ — 532

- 7.1 Introduction — **532**
- 7.2 Setting up the SimCoupler — **532**
- 7.3 Preparing the PSIM model — **535**
- 7.4 Preparing the Simulink model — **539**

Chapter 8

SmartCtrl — 546

- 8.1 Introduction — **546**
- 8.2 Power stage of the converter — **546**
- 8.3 Obtaining the frequency response of the power stage — **550**
- 8.4 Designing the controller — **552**
- 8.5 Parameters of designed controller — **560**
- 8.6 Exporting the parameters of designed controller — **561**
- 8.7 Addition of the controller to the power stage — **563**

- 8.8 Testing the controller — **570**
- 8.9 Designing with another type of controller — **573**
- 8.10 Automatic design of power stage and controller — **579**
- 8.11 Controller design for common type of DC–DC converters — **582**
- 8.12 Sample designs for SmartCtrl — **589**

References for further study — 591

Index — 593