

Contents

Preface11

Chapter 1 • The Arduino Uno R412

1.1 Overview12

1.2 The Arduino Uno R4 against Uno R313

1.3 The Arduino Uno R4 Minima hardware15

1.4 The Arduino Uno R4 Projects Kit20

Chapter 2 • Arduino Uno R4 Program Development23

2.1 Overview23

2.2 Installing the Arduino IDE 2.1.024

2.3 Software-only programs26

2.3.1 Example 1: Sum of integer numbers26

2.3.2 Example 2: Table of squares29

2.3.3 Example 3: Volume of a cylinder30

2.3.4 Example 4: Centigrade to Fahrenheit31

2.3.5 Example 5: Times table33

2.3.6 Example 6: Table of trigonometric sine34

2.3.7 Example 7: Table of trigonometric sine, cosine and tangent36

2.3.8 Example 8: Integer calculator37

2.3.9 Example 9: Dice40

2.3.10 Example 10: Floating point calculator41

2.3.11 Example 11: Binary, octal, hexadecimal43

2.3.12 Example 12: String functions44

2.3.13 Example 13: Initializing an array46

2.3.14 Example 14: Character functions48

2.3.15 Example 15: Solution of a quadratic equation50

2.3.16 Example 16: Lucky day of the week53

2.3.17 Example 17: Factorial of a number54

2.3.18 Example 18: Add two square matrices56

Chapter 3 • Hardware Projects with LEDs59

3.1 Overview59

3.2 Project 1: Blinking LED – using the on-board LED	59
3.3 Project 2: Blinking LED – using an external LED	60
3.4 Project 3: LED flashing SOS	63
3.5 Project 4: Alternately blinking LEDs	64
3.6 Project 5: Chaser-LEDs	67
3.7 Project 6: Chasing LEDs 2	70
3.8 Project 7: Binary counting LEDs	72
3.9 Project 8: Random flashing LEDs - Christmas lights	74
3.10 Project 9: Button controlled LED	75
3.11 Project 10: Controlling the LED flashing rate - external interrupts	80
3.12 Project 11: Reaction timer	83
3.13 Project 12: LED color wand	85
3.14 Project 13: RGB fixed colors	87
3.15 Project 14: Traffic lights	89
3.16 Project 15: Traffic lights with pedestrian crossings	94
3.17 Project 16: Using the 74HC595 shift register – binary up counter	100
3.18 Project 17: Using the 74HC595 shift register - random flashing 8 LEDs	103
3.19 Project 18: Using the 74HC595 shift register - chasing LEDs	104
3.20 Project 19: Using the 74HC595 shift register - turn ON a specified LED	105
3.21 Project 20: Using the 74HC595 shift register - turn ON specified LEDs	107
Chapter 4 • 7-Segment LED Displays	109
4.1 Overview	109
4.2 7-Segment LED display structure	109
4.3 Project 1: 7-Segment 1-digit LED counter	111
4.4 Project 2: 7-Segment 4-digit multiplexed LED display	114
4.5 Project 3: 7-Segment 4-digit multiplexed LED display counter - timer interrupts	119
4.6 Project 4: 7-Segment 4-digit multiplexed LED display counter - blanking leading zeroes	124
4.7 Project 5: 7-Segment 4-digit multiplexed LED display - reaction timer	128
4.8 Project 6: Timer interrupt blinking on-board LED	133
Chapter 5 • Liquid Crystal Displays	136
5.1 Overview	136

5.2 The I ² C bus.	136
5.3 I ² C ports of the development board	137
5.4 I ² C LCD	137
5.5 Project 1: Display text on the LCD	140
5.6 Project 2: Scrolling text on the LCD	142
5.7 Project 3: Display custom characters on the LCD.	144
5.8 Project 4: LCD based conveyor belt goods counter.	145
5.9 Project 5: LCD based accurate clock using timer interrupts.	149
5.10 Project 6: LCD dice	154

Chapter 6 • Sensors157

6.1 Overview	157
6.2 Project 1: Analog temperature sensor	157
6.3 Project 2: Voltmeter.	160
6.4 Project 3: On/off temperature controller.	161
6.5 Project 4: Darkness reminder – using a light-dependent resistor (LDR)	164
6.6 Project 5: Tilt detection	167
6.7 Water level sensor.	169
6.7.1 Project 6: Displaying water level.	169
6.7.2 Project 7: Water level controller	172
6.7.3 Project 8: Water flooding detector with buzzer	174
6.8 Project 9: Sound detection sensor — control the relay by clapping hands.	175
6.9 Project 10: Flame sensor - fire detection with relay output.	177
6.10 Project 11: Temperature and humidity display.	180
6.11 Project 12: Generating musical tones - melody maker	184

Chapter 7 • The RFID Reader187

7.1 Overview	187
7.2 Project 1: Finding the Tag ID	187
7.3 Project 2: RFID door lock access with relay.	190

Chapter 8 • The 4x4 Keypad194

8.1 Overview	194
8.2 Project 1: Display the pressed key code on the Serial Monitor.	195
8.3 Project 2: Integer calculator with LCD	198

8.4 Project 3: Keypad door security lock with relay	203
Chapter 9 • The Real-Time Clock (RTC) Module	207
9.1 Overview	207
9.2 The supplied RTC module	207
9.3 Project 1: RTC with Serial Monitor	207
9.4 Project 2: RTC with LCD	211
9.5 Project 3: Temperature and humidity display with time stamping	213
9.6 Using the built-in RTC	216
9.6.1 Project 4: Setting and displaying the current time	216
9.6.2 Project 5: Periodic interrupt every 2 seconds	218
Chapter 10 • The Joystick.	221
10.1 Overview	221
10.2 The joystick	221
10.3 Project 1 - Reading analog values from the joystick	221
Chapter 11 • The 8×8 LED Matrix.	226
11.1 Overview	226
11.2 The supplied 8×8 LED matrix	226
11.3 Project 1: Displaying shapes	227
Chapter 12 • Motors: Servo and Stepper	231
12.1 Overview	231
12.2 The servo motor	231
12.2.1 Project 1: Test-rotate the servo	232
12.2.2 Project 2: Servo sweep	234
12.2.3 Project 3: Joystick-controlled servo	235
12.3 The stepper motor	237
12.3.1 Project 4: Rotate the motor clockwise and then anticlockwise.	238
Chapter 13 • The Digital To Analog Converter (DAC).	241
13.1 Overview	241
13.2 Project 1: Generating a square wave with 2 V amplitude	241
13.3 Generating sine wave – using the analogWave library	242
13.3.1 Project 2: Generate a sine wave	243

13.3.2 Project 3: Sine wave sweep frequency generator	244
13.3.3 Project 4: Generate sine wave whose frequency changes with potentiometer. .	245
13.3.4 Project 5: Generate a square wave with frequency of 1 kHz and amplitude of 1 V	247
Chapter 14 • Using the EEPROM, the Human Interface Device, and PWM	248
14.1 Overview	248
14.2 The EEPROM memory.	248
14.3 Human Interface Device (HID)	249
14.4 Project 1: Keyboard control to launch Windows programs.	250
14.5 The Pulse Width Modulation (PWM)	253
14.5.1 PWM channels of the Arduino Uno R4	255
14.5.2 Project 2: LED dimming using PWM.	255
Chapter 15 • The Arduino Uno R4 WiFi	257
15.1 Overview	257
15.2 The LED matrix	260
15.2.1 Project 1: Using LED matrix 1 - creating a large + shape.	260
15.2.2 Project 2: Creating images by setting bits	262
15.2.3 Project 3: Using LED matrix 2 - creating a large + shape.	265
15.2.4 Project 4: Animation - displaying a word	267
15.3 Using the WiFi	269
15.3.1 UDP and TCP	269
15.3.2 UDP communication	270
15.3.3 TCP communication.	271
15.3.4 Project 5: Controlling the Arduino Uno R4 WiFi on-board LED from a smartphone using UDP	272
15.4 Bluetooth	276
15.4.1 Bluetooth BLE.	277
15.4.2 Bluetooth BLE Software Model	278
Chapter 16 • Serial Communications	280
16.1 Overview	280
16.2 Project 1: Receiving ambient temperature from an Arduino Uno R3	281
Chapter 17 • Using an Arduino Uno Simulator	285

17.1 Why simulation?	285
17.2 The Wokwi simulator	286
17.2.1 Project 1: A simple project simulation - flashing LED.	287
17.2.2 Project 2: Displaying text on LCD	288
17.2.3 Project 3: LCD seconds counter	290
Chapter 18 • The CAN bus	292
18.1 Overview	292
18.2 The CAN bus	292
18.2.1 CAN bus termination	292
18.2.2 CAN bus data rate.	294
18.2.3 Cable stub length	295
18.2.4 CAN bus node.	295
18.2.5 CAN bus signal levels	296
18.2.6 CAN_H voltage	297
18.2.7 The CAN_L voltage	297
18.2.8 Bus arbitration	297
18.2.9 Bus transceiver.	297
18.2.10 CAN connectors	298
18.3 Arduino Uno R4 CAN bus interface.	300
18.3.1 CAN bus transceivers.	300
18.4 Project 1: Arduino Uno R4 WiFi to Arduino Uno R4 Minima CAN bus communication	301
18.5 Project 2: Sending the temperature readings over the CAN bus.	306
Chapter 19 • Infrared Receiver and Remote Controller	311
19.1 Overview	311
19.2 The supplied infrared receiver	311
19.3 The supplied infrared remote control transmitter unit.	311
19.4 Operation of an infrared remote control system.	312
19.5 Project 1: Decoding the IR remote control codes	314
19.6 Project 2: Remote relay activation/deactivation.	317
19.7 Project 3: Infrared remote stepper motor control.	320
Index	325